

# Transimpedance Amplifiers (TIA): Choosing the Best Amplifier for the Job

Hooman Hashemi

## ABSTRACT

This application note is intended as a guide for the designer looking to amplify the small signal from a photodiode or avalanche diode so that it would be large enough for further processing (e.g. data acquisition) or to trigger some other event in a system. The challenge in doing so, as always, is to not degrade the signal such that it becomes indistinguishable from random noise and to maintain enough signal bandwidth so that “information” is preserved. We will present some ideas on this and develop analysis and optimization techniques, as well as list the devices with the most desirable specifications for such applications.

## Contents

1	General Considerations .....	1
2	Equivalent Input Noise Source Modeling .....	3
3	Optimizing the Device Choice and Operation .....	4
4	Post Amplification Effect on SNR .....	5
5	Summary .....	6

## List of Figures


1	Basic TIA Configuration Using and Ultra-Low Noise Device (LMH6629) .....	2
2	TIA Compensation Capacitor ( $C_F$ ) and Subsequent Bandwidth ( $f_{-3dB}$ ) .....	2
3	Transimpedance Amplifier Equivalent Input Source ( $i_{ni}$ ) Model .....	3
4	Block Diagram of Entire Signal Path to Compute Overall SNR .....	5

## List of Tables

1	Different Amplifier Candidates Optimized Setting Compared Side-by-Side .....	4
---	--	---

## 1 General Considerations

As it turns out, selecting the best operational amplifier to interface to the photodiode is a juggling act between many parameters, some significant while others less so; for now, suffice to say that the lowest noise voltage device is *not always* the winner. We will discuss the tradeoffs further in this document.

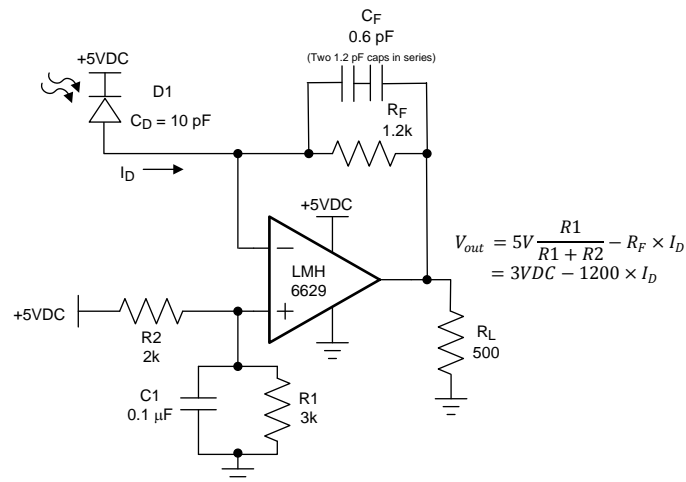

**Figure 1. Basic TIA Configuration Using and Ultra-Low Noise Device (LMH6629)**

Often times, the transducer (Photodiode) is chosen based on its form factor or electrical characteristics and the following need to be determined:

- How much gain is needed?
- What bandwidth has to be achieved?
- What is the highest noise than can be tolerated?

In most cases, since the photodiode signal is usually very small, the 1st TIA stage is followed by subsequent gain stage(s) to optimize the balance between noise and bandwidth. Photodiode manufacturers specify how much current can be generated for a certain incident light power. A large area photodiode produces more current in response to incident light, at the expense of higher capacitance (and hence lower speed).

So, knowing the final voltage level desired, based on the specifics of what needs to be driven (e.g. input of ADC, logic gate, etc.), the “total” signal path gain can be nailed down. Set the 1<sup>st</sup> Transimpedance stage gain too high, and you will limit the attainable bandwidth for the signal spectrum at hand. On the other hand, not enough gain degrades SNR and leaves you with too much gain to make up for and unnecessary cost, complexity, and possible signal degradation. Inherent in the question of the what gain to run the 1<sup>st</sup> stage, is the second order effect of the photodiode capacitance causing excessive noise gain increase at the higher frequencies (more on that later).

The equations in Figure 2 define the value of the compensation capacitor ( $C_F$ ) as a function of the Operational Amplifier Gain Bandwidth Product (GBWP), Transimpedance gain ( $R_F$ ), and the total input capacitance ( $C_{IN}$ ) where:

$$C_{IN} = C_D + C_{CM} + C_{DIFF} \quad (1)$$

where:

- $C_D$  : Photodiode capacitance
- $C_{CM}$  : Amplifier common mode capacitance (each input to ground)
- $C_{DIFF}$  : Amplifier differential mode capacitance (across the inputs)

**Optimum CF Value:**

$$C_F = \sqrt{\frac{C_{IN}}{2\pi(GBWP)R_F}}$$

**Resulting -3dB Bandwidth:**

$$f_{-3dB} \cong \sqrt{\frac{GBWP}{2\pi R_F C_{IN}}}$$


**Figure 2. TIA Compensation Capacitor ( $C_F$ ) and Subsequent Bandwidth ( $f_{-3dB}$ )**

The attainable -3dB bandwidth ( $f_{-3dB}$ ) can also be inferred from [Figure 2](#).

## 2 Equivalent Input Noise Source Modeling

The highest noise that can be tolerated should be at least a few dB lower than the smallest signal present.

It is a common technique to utilize noise analysis, using hand calculation or alternatively a simulation tool such as TINA-TI, on the entire signal path in order to make sure the noise level is below this limit. Often times, this is done with "input referred noise" modeled as a noise source next to the input such that it is possible to directly compare the signal and the noise level with each other. Refer to [Figure 3](#) for the depiction of this input referred source " $i_{ni}$ ".

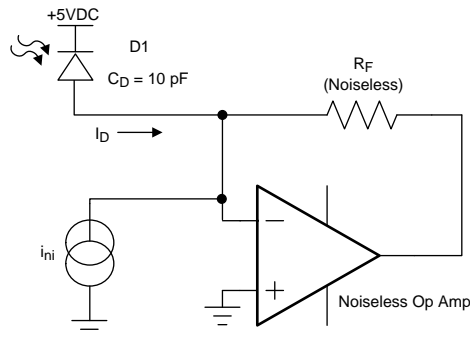

**Figure 3. Transimpedance Amplifier Equivalent Input Source ( $i_{ni}$ ) Model**

Referring all noise sources to the input allows immediate SNR evaluation and highlights the "dominant noise" source, which can be an effective tool in any attempt at improving SNR by tackling the most offensive noise source(s).

The expression for  $i_{ni}$  is derived within the "[Transimpedance Considerations for High-Speed Amplifiers](#)" (shown as " $i_{EQ}$ ") and copied below for reference:

$$i_{ni} = \sqrt{i_n^2 + \left(\frac{e_n}{R_F}\right)^2 + \frac{4kT}{R_F} + \frac{(e_n 2\pi f_{-3dB} C_{IN})^2}{3}} \quad (2)$$

Where:

- $i_n$  = inverting input spot current noise
- $4kT = 16.4 \times 10^{-21} \text{ J}$  at room temperature
- $R_F$  = feedback resistor
- $e_n$  = non-inverting input spot voltage noise
- $C_{IN}$  = Total inverting input total capacitance. See [Equation 1](#)
- $f_{-3dB}$  = noise integration frequency limit

The contributing terms to input referred noise current ( $i_{ni}$ ) in Equation 2 are:

a) Noise Current Term:

$$i_n \quad (3)$$

b) Noise Voltage Term:

$$e_n / R_F \quad (4)$$

c) Thermal Noise Term:

$$\sqrt{\frac{4kT}{R_F}} \quad (5)$$

where  $4kT = 16.4 \times 10^{-21} \text{ J}$  at room temperature

d) Input Capacitance Term:

$$\frac{e_n 2\pi f_{-3dB} C_{IN}}{\sqrt{3}} \quad (6)$$

While most of the terms shown may be self-explanatory, the last term needs to be described. This term is the result of the noise increase caused by the presence of the total inverting input capacitance ( $C_{IN}$ ), which has the net effect of increasing Noise Gain beyond a certain frequency set by  $R_F$  and  $C_{IN}$ .

The overall SNR can be optimized by the proper choice of operational amplifier, selected gain, and the total signal path gain. With several cascaded stages, it is desirable to take the highest gain at the earliest stage and to minimize its noise contribution since it has the highest impact on SNR. So, for the 1<sup>st</sup> stage, choose the best operational amplifier (by using the analysis method developed here) while operating at the highest Transimpedance gain possible which still allows the entire spectrum of interest to pass.

### 3 Optimizing the Device Choice and Operation

For a given operational amplifier GBWP, use the expression in Figure 2 to pick the highest gain ( $R_F$ ) that achieves the required bandwidth. If this  $R_F$  value causes excessive swing at maximum signal, set  $R_F$  to what the maximum signal and voltage swing dictates. A spreadsheet is a good tool to use so that you can evaluate many possible device options side-by-side, given their datasheet specifications and application operating conditions. Next, use the  $i_{ni}$  expression in Equation 2 to compute the equivalent input referred noise current and determine if the resulting SNR is adequate for the application at hand. To improve SNR, select a different operational amplifier to try and maximize SNR as much as possible. The individual noise sources in (Equation 3 through Equation 6) can point out which noise source is dominant and should therefore be targeted for reduction to have the maximum impact on SNR.

Let's take an example photodiode and try to find the best amplifier to be used with it while considering all input referred noise sources described earlier:

Example:

- Total input capacitance  $C_{IN}$ : 10pF. Note: Device input capacitance not considered (assumed  $C_{IN} = C_D$ )
- Photodiode signal range: 10nA (Min) to 1uA (Max)
- Required Bandwidth: 80MHz
- Required swing with minimum signal: 1mV

Following the procedure above, and comparing some possible device candidates for the 1<sup>st</sup> stage amplification, here is what you get:

**Table 1. Different Amplifier Candidates Optimized Setting Compared Side-by-Side**

Device <sup>(1)</sup>	GBWP (MHz) <sup>(2)</sup>	$i_n$ (pA / RtHz) <sup>(2)</sup>	$e_n$ (nV / RtHz) <sup>(2)</sup>	$R_F$ (Ohm) <sup>(3)</sup>	Noise Current Term (pA / RtHz) <sup>(4)</sup>	Noise Voltage Term (pA / RtHz) <sup>(4)</sup>	Thermal Noise Term (pA / RtHz) <sup>(4)</sup>	Input Capacitance Term (pA / RtHz) <sup>(4)</sup>	SNR (dB) <sup>(5)</sup>	Post Amp Gain (dB) <sup>(6)</sup>
<a href="#">THS4631</a>	325	0.002	7	810	0.002	8.7	4.5	20.3 <sup>(7)</sup>	53	42
<a href="#">LMH6629</a>	4,000	2.6	0.69	10k	2.6 <sup>(7)</sup>	0.07	1.3	2 <sup>(7)</sup>	69	20
<a href="#">OPA657</a>	1,600	0.0013	4.8	3.9k	0.0013	1	2	14 <sup>(7)</sup>	57	28

<sup>(1)</sup> Device input capacitance not considered (assumed  $C_{IN} = C_D$ )

<sup>(2)</sup> Datasheet parameter

<sup>(3)</sup> Selected to meet bandwidth required using Figure 2

<sup>(4)</sup> Computed using Equation 2

<sup>(5)</sup> SNR computed as ratio of minimum signal (10nA) to input referred spot noise  $i_{ni}$  [= 20 \* log(10nA /  $i_{ni}$ ) ]

<sup>(6)</sup> For 1mV final signal with minimum signal


<sup>(7)</sup> Dominant term

Table 1 results show that the [LMH6629](#) delivers the highest SNR for this application by virtue of its ultra-low input noise voltage ( $e_n$ ) which is low enough to be a non-factor and also results in a minimal "input capacitance term" as well. In the end, which amplifier gives the best SNR is determined by the specifics of the application or operating conditions and the determining factor depends which of the noise terms dominates. Notice that one must weigh the benefit of the highest SNR against cost, and also the additional post amp gain needed. The small  $R_F$  value for [THS4631](#), and the subsequent large post amp gain it

needs, might prohibit this device's application in this particular example. A very important thing to note is that the FET input devices (e.g. [THS4631](#), [OPA657](#), etc.) not only have an inherent noise current advantage over BJT input devices (e.g. [LMH6629](#), etc.), but they also reduce the output offset error that arises from their near zero input bias current working against the feedback resistor  $R_F$ . If the operating conditions of this example were different, one might very well end up with a situation where low noise current sets the attainable SNR and thus it would be more appropriate to select a FET input device instead.

#### 4 Post Amplification Effect on SNR

To demonstrate how SNR is affected when the 1<sup>st</sup> TIA stage is followed by additional non-ideal (noisy) amplifiers to increase signal amplitude to what is needed, let's consider an example shown in [Figure 4](#). In this example, the [LMH6629](#) 1<sup>st</sup> stage from [Table 1](#) is chosen along with a cascade of 6dB voltage gain stages having a NF of 10dB each as post amp. To get 20dB total post amp voltage gain needed, we must use more than 3 cascaded stages. Four cascaded stages are shown in the example below:

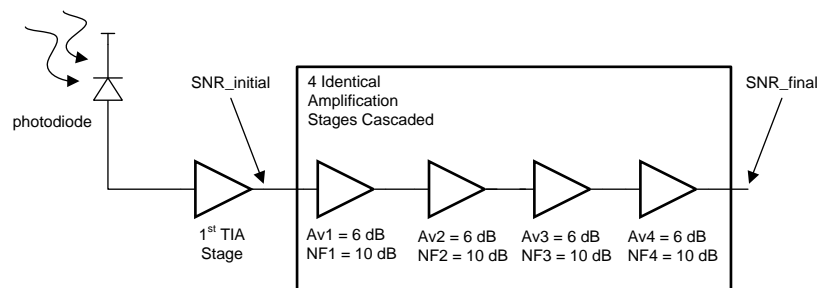

**Figure 4. Block Diagram of Entire Signal Path to Compute Overall SNR**

The post amp consists of a series of identical cascaded stages of voltage gain ( $A_v$ ) and Noise figure (NF) each.

Here is the overall Noise Factor (F) expression (known as "Friss Formula") at the post amp output using Power Gain ( $G_n$ ) and Noise Factor ( $F_n$ ) of the n stages:

$$F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \frac{F_4 - 1}{G_1 G_2 G_3} + \dots + \frac{F_n - 1}{G_1 G_2 G_3 \dots G_{n-1}} \quad (7)$$

Knowing the entire signal path Noise Figure ( $NF = 10 \cdot \log(F)$ ), one can compute the resulting  $SNR_{final}$  with  $SNR_{initial}$  known (69dB in this case from the [Table 1](#) entry for the [LMH6629](#)):

$$SNR_{final} = SNR_{initial} - NF \quad (8)$$

Let's compute G and F from  $A_v$  and NF given:

$$G_1 = G_2 = G_3 = G_4 = [10^{(A_v / 20)}]^2 = [10^{(6 / 20)}]^2 = (2)^2 = 4 \text{ (V}^2/\text{V}^2\text{)} \quad (9)$$

$$F_1 = F_2 = F_3 = F_4 = 10^{(NF / 10)} = 10^{(10 / 10)} = 10 \text{ (V}^2/\text{V}^2\text{)} \quad (10)$$

From [Equation 7](#):

$$F = 10 + (10-1) / 4 + (10-1) / 4^2 + (10-1) / 4^3 = 13 \quad (11)$$

Computing NF from knowing F:

$$NF = 10 * \log(13) = 11.1\text{dB} \quad (12)$$

From [Equation 8](#):

$$SNR_{final} = SNR_{initial} - NF = 69\text{dB} - 11.1\text{dB} = 57.9\text{dB} \quad (13)$$

## 5 Summary

This application note developed some insight into the parameters that affect the TIA most in terms of bandwidth and noise and demonstrated with examples how to compute SNR, and optimize it which in turn allows one to find the most suitable amplifier to use for the 1st TIA stage. Furthermore, the impact of additional amplification on overall SNR was analyzed and evaluated numerically such that the user can keep track of the noise in order to successfully specify and build an optimized photodiode amplifier system.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)